

Digital Electronics

Circuit Example: Four-Bit Serial-To-Parallel Converter

S Le Goff

June 2026

5. Four-bit serial-to-parallel converter

Design of a serial-to-parallel converter. This circuit converts an input bit stream with a bit rate of N bits/second into four output bit streams with bit rates of $N/4$ bits/second each.

