

Digital Electronics


Circuit Example: A Four-Bit Counter

S Le Goff

June 2026

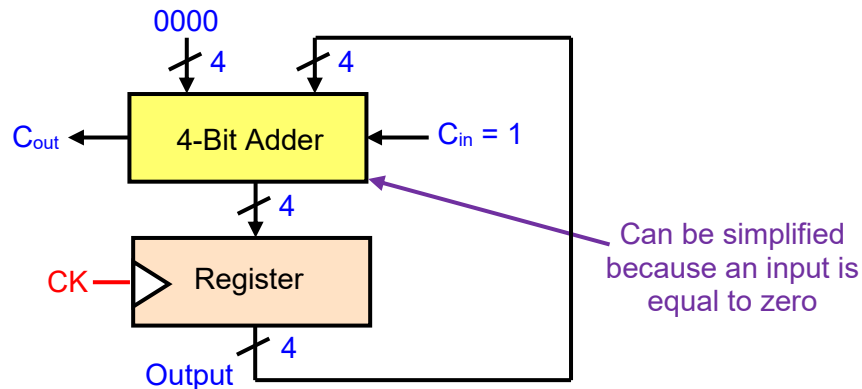
1. Four-bit counter

Design of a four-bit counter designed using a four-bit adder and a four-bit register. It has the advantage of being very simple to design and understand.



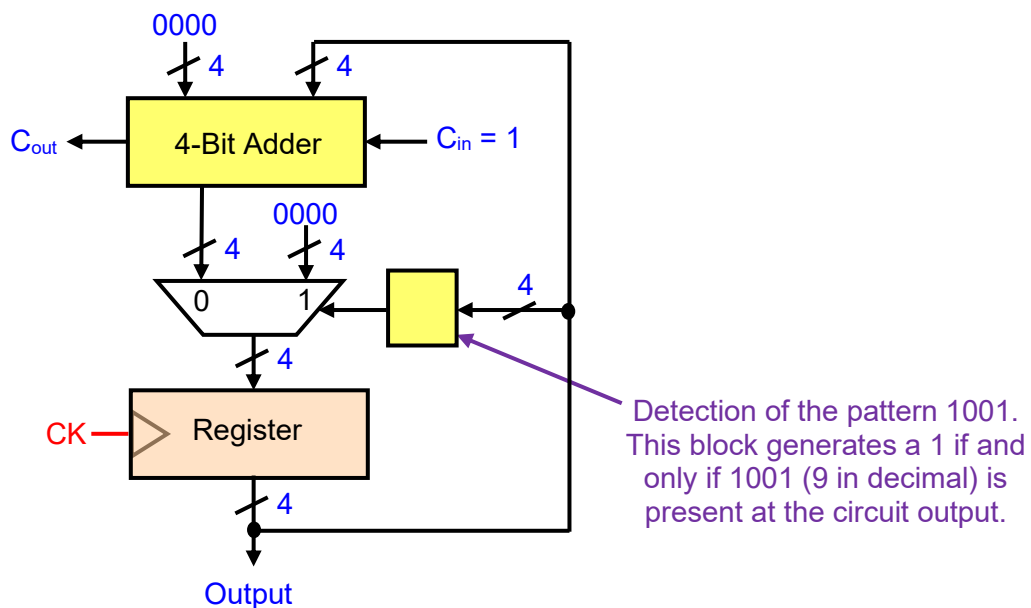2. Four-bit decimal counter

Design of a decimal counter based on the design shown above (circuit A). A decimal counter counts from 0 to 9, and back to zero.



A more detailed logic diagram for the four-bit decimal counter:

